

Tribhuvan University
Institute of Science and Technology
2073

Bachelor Level/ First Year/ First Semester/ Science
Computer Science and Information Technology (CSc. 111)
(Digital Logic)

Full Marks: 60
Pass Marks: 24
Time: 3 hours.

Candidates are required to give their answers in their own words as far as practicable.
The figures in the margin indicate full marks.

Long Questions:

Attempt any two questions: (2 × 10=20)

1. Explain the magnitude comparator and also design a logic diagram for 4 bit magnitude comparator.
2. What do you mean by decoder? Design a 3 to 8 line decoder using 2 to 4 line decoder and explain it.
3. What do you mean by ripple counter? Explain the design procedure of sequential circuits.

Short Questions:

Attempt any eight questions: (8 × 5=40)

4. Convert the following hexadecimal number to decimal and octal numbers.
 - a) 4FF
 - b) 6FED
5. Explain the error detection code with example.
6. Explain the duality theorem with example.
7. Design half adder logic circuit using only universal gates.
8. Draw a logic circuit of 8*1 multiplexer.
9. Design the 4 bit parallel binary adder.
10. Explain the PLA with the block diagram.
11. Explain the R-S flip flop with truth table.
12. Explain the shift register with example.
13. Write short note on (any two):
 - a) Binary counter
 - b) State reduction
 - c) Negative edge triggering